



Verilog Project

Simple Single Cycle RISC_V

Submitted by: AbdelRahman Atef Eid Yassin Yousef

Track: Digital IC Design

Supervisor: TA\ Fayza

Date of submission : 16/8/2023

Objective:

Design and implement RISC V Single Cycle processor which can execute some simple reduced Instruction set .

Problem Statement:

Implement a single cycle 32-bit RISC V processor using Verilog language that can execute a stored program, which consists of some simple reduced Instruction set architecture. The Design should be able to execute the instruction in just one clock cycle .

Design & Implementation

Main Design

The main design is implemented in file attached RISC_v.v which implement the schematic diagram below.

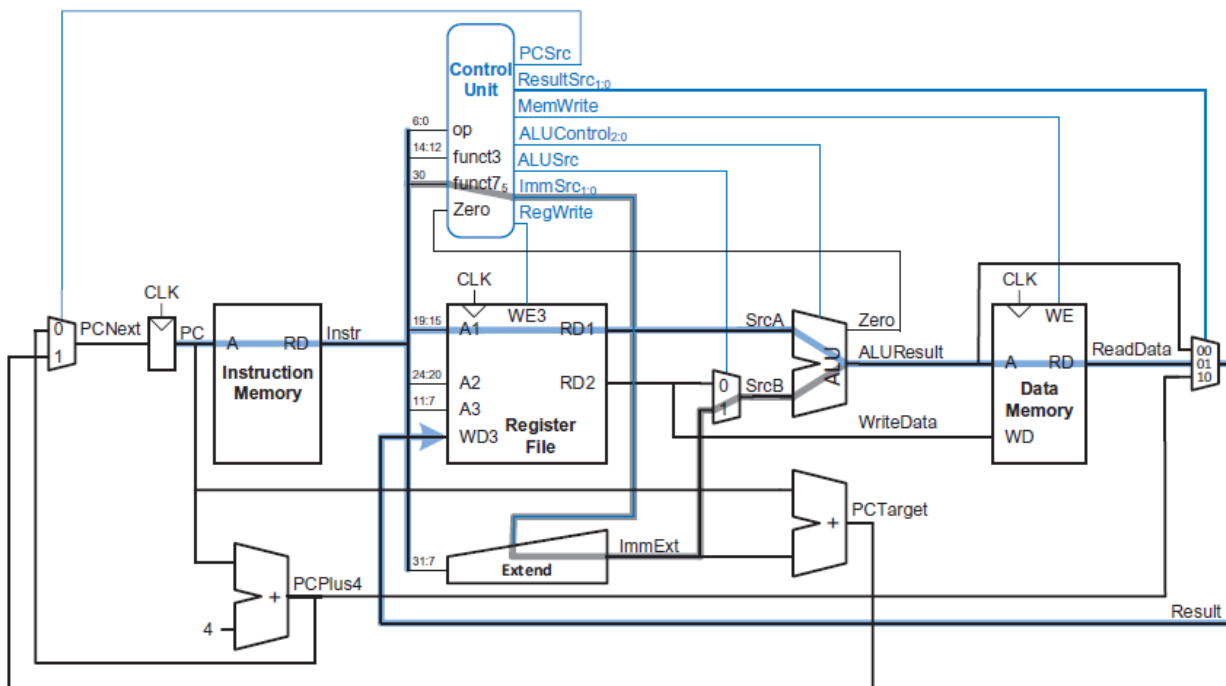


Figure 7.17 Critical path for 1w

The Structural Design consists of many smaller components:

- 1- PC (Program Counter to store address of current instruction executed)
- 2- Instruction Memory (Store Program to be executed)
- 3- Register File (store variables we want to use)
- 4- ALU (performs arithmetic and logic operations)
- 5- Data Memory (large storage than reg file)
- 6- Immediate extender (extend sign bit to allow negative numbers evaluation)
- 7- Muxs (choose the inputs to alu and pc)
- 8- Control Unit (Controls interconnection between All Component)

Instruction Set Architecture

Our design supports the following reduced instruction set :

Instruction	Type	illustration
Add \$s1,\$s2,\$s3	R Type	Addition of two numbers
Sub \$s1,\$s2,\$s3		Subtraction of two numbers
Or \$s1,\$s2,\$s3		Oring logic operation of two numbers
And \$s1,\$s2,\$s3		Anding logic operation of two numbers
SLT \$s1,\$s2,\$s3		If $s2 < s3$ set $s1$ by 1
Addi \$s1,\$s2,5	I type	Immediate Addition
Andi \$s1,\$s2,5		Immediate Anding
Ori \$s1,\$s2,5		Immediate Oring
Slti \$s1,\$s2,5		Immediate Set less than
Lw \$s1,4(\$s2)	S type	Load value from memory to register
Sw \$s1,4(\$s2)		Store value from register to memory
Jal rd,immediate	J Type	Jump to a block of program and save next instruction to a register to return to it

Components of the design

1- PC


A program Counter register which holds current instruction address which is 32 bit wide is implemented in **PC.v** which gets a new address each clock positive edge .

A mux is used to choose address of PC+4 or branch address

2- Instruction Memory

An Instruction memory of 256 location for testing which each location has 4 byte word of 32 bit . Each location is denoted by 32 bit Address in multiple of 4 .

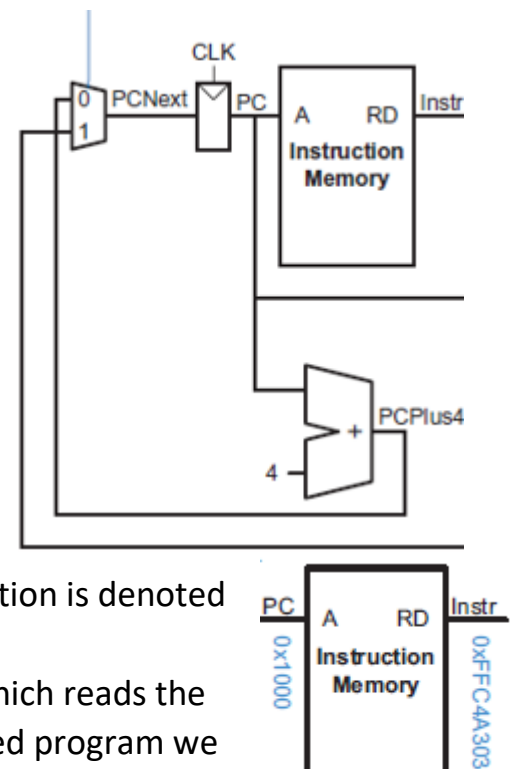Memory is implemented in file Instruction_Memory.v which reads the instructions in file mymem2.dat which contains the stored program we want to execute in hexadecimal notation .




```

mymem2.dat - No
memory_instructions_illustrations.txt - Notepad
File Edit Format View Help
002081B3 // add $3, $1, $2
403202B3 // sub $5, $4, $3
00808383 // lw $7, 8($1)
0013F333 // and $6, $1, $7
0080c623 // sw $8,12($1)
001122B3 // slt $5, $2, $1
00210463 // beq $2, $2, 8 // 8 is offset
002081B3 // add $3, $1, $2
002081B3 // add $3, $1, $2
00110293 // addi $5, $2, 1
00B564B3 // OR $9,$10,$11
00312293 // slti $5, $2, 3
00517293 // andi $5, $2, 5
0056E793 // ori $15,$13,5
  
```

3- Control Unit

A control unit implemented in file Control_Unit.v which has two main components

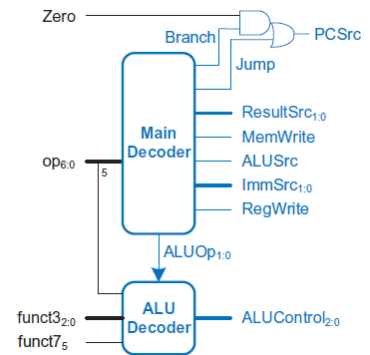- 1- Main Decoder : Responsible for generating all control signals of other components implemented in file Main_Decoder.v
- 2- ALU Decoder : Responsible for generating control signals for ALU implemented in file ALU_Decoder.v



Control Unit is responsible for decoding instruction to tell other components what to do.

Main Decoder Truth Table :

Instruction	Opcode	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
lw	0000011	1	00	1	0	01	0	00	0
sw	0100011	0	01	1	1	xx	0	00	0
R-type	0110011	1	xx	0	0	00	0	10	0
beq	1100011	0	10	0	0	xx	1	01	0
I-type ALU	0010011	1	00	1	0	00	0	10	0
j al	1101111	1	11	x	0	10	0	xx	1

ALU Decoder Truth Table :

Table 7.3 ALU Decoder truth table


ALUOp	funct3	{op ₅ , funct _{7:5} }	ALUControl	Instruction
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add
	000	11	001 (subtract)	sub
	010	x	101 (set less than)	slt
	110	x	011 (or)	or
	111	x	010 (and)	and

4- Register File

A 32 locations of 32 bits wide register file is implemented in **REG_FILE.v** . Read operation doesn't depend on clock but the address of A1 and A2 are put on the output . Write Operation is synchronous with clock .

Table 6.1 RISC-V register set

Name	Register Number	Use
zero	x0	Constant value 0
ra	x1	Return address
sp	x2	Stack pointer
gp	x3	Global pointer
tp	x4	Thread pointer
t0-2	x5-7	Temporary registers
s0/ fp	x8	Saved register/Frame pointer
s1	x9	Saved register
a0-1	x10-11	Function arguments/Return values
a2-7	x12-17	Function arguments
s2-11	x18-27	Saved registers
t3-6	x28-31	Temporary registers

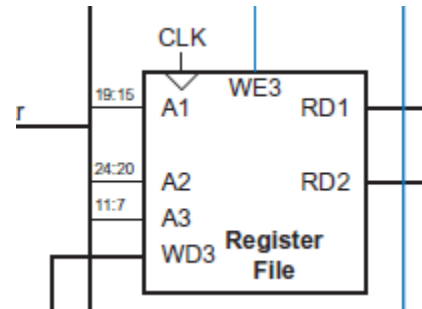

5- Immediate Extender

It is implemented in **Immediate_extender.v** which is responsible for extending the sign of branch address to match 32 bit address we deal with . It is implemented according to truth table :

ImmSrc	ImmExt	Type	Description
00	{{20{Instr[31]}}, Instr[31:20]}	I	12-bit signed immediate
01	{{20{Instr[31]}}, Instr[31:25], Instr[11:7]}	S	12-bit signed immediate
10	{{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0}	B	13-bit signed immediate
11	{{12{Instr[31]}}, Instr[19:12], Instr[20], Instr[30:21], 1'b0}	J	21-bit signed immediate

6- ALU


It is implemented in file **ALU.v** which does the Arithmetic and logic operations according to truth table below :

ALUOp	funct3	{op5, funct7s}	ALUControl	Instruction
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add
	000	11	001 (subtract)	sub
	010	x	101 (set less than)	slt
	110	x	011 (or)	or
	111	x	010 (and)	and

7- Data Memory

A Data Memory also implemented in **Data_Memory.v** which has asynchronous read operation according to 32 bit address location which is also should be multiple of 4 as each word in memory is 32 bit wide (4 bytes) .

 It has a synchronous write signal with the positive edge of the clk.



Simulation Results

Tables below explains how the program executes

A register file initialized with hex values inside file myreg.dat

Data Memory initialized with hex values in file mydmem.dat

1	00000000
2	00000001
3	00000002
4	00000003
5	00000004
6	00000005
7	00000006
8	00000007

Figure 2 Data Memory Data

1	0
2	4
3	10
4	12
5	18
6	20
7	24
8	28
9	30
10	32
11	34
12	32
13	30
14	28
15	26
16	24
17	28
18	30
19	32
20	34
21	30
22	80
23	90
24	60
25	70
26	50
27	40
28	31
29	20
30	22
31	24
32	37

Figure 1 Reg
initialization

A table below summarizes the expected output to each instruction

Instruction	Effect on next clock cycle
add \$3, \$1, \$2	\$3 = 14h
sub \$5, \$4, \$3	\$5 = 04h
lw \$7, 8(\$1)	\$7 = 03h
and \$6, \$1, \$7	\$6 = 4h and 12h = 0
sw \$8, 12(\$1)	Location number 4 in memory = 30h
slt \$5, \$2, \$1	\$5 = 0
beq \$2, \$2, 8 // 8 is offset to label l1	Pc =
add \$3, \$1, \$2	skipped
L1:add \$3, \$1, \$2	\$3 = 14h
addi \$5, \$2, 1	\$5 = 11h
OR \$9, \$10, \$11	\$9 = 34 h or 32h = 36h
slti \$5, \$2, 3	\$5 = 0
andi \$5, \$2, 5	\$5 = 10h and 5 = 0
ori \$15, \$13, 5	\$15 = 28 h or 5 = 2dh

A simulation wave form is taken below and we check the values on register and memory if executes the program

